


# Lesson 3

# Multiplexer (MUX)

# Multiplexer (MUX), or Selector

- Selects one of the  $N$  inputs to connect it to the output
  - based on the value of a  $\log_2 N$ -bit control input called select
- Example: 2-to-1 MUX

$S$	$Y$
0	$D_0$
1	$D_1$

 


$S$	$D_1$	$D_0$	$Y$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

# Multiplexer (MUX), or Selector (II)

- Selects one of the  $N$  inputs to connect it to the output
  - based on the value of a  $\log_2 N$ -bit control input called select
- Example: 2-to-1 MUX

- $S=1$

 - $A \text{ AND } 0 = 0$
- $B \text{ AND } 1 = B$
- $B \text{ OR } 0 = B$




- $S=0$

- $A \text{ AND } 1 = A$
- $B \text{ AND } 0 = 0$
- $A \text{ OR } 0 = A$

# Multiplexer (MUX), or Selector (III)

- The output C is always connected to either the input A or the input B
  - Output value depends on the value of the **select line S**

<b>S</b>	<b>C</b>
0	A
1	B


 


## Example (10 min):

- Draw the schematic for a 4-input (4:1) MUX
  - Gate level: as a combination of basic AND, OR, NOT gates and simulate it in the [logic.ly](https://www.logic.ly)
  - Module level: As a combination of 2-input (2:1) MUXes

# Aside: Logic Using Multiplexers


- Multiplexers can be used as lookup tables to perform logic functions

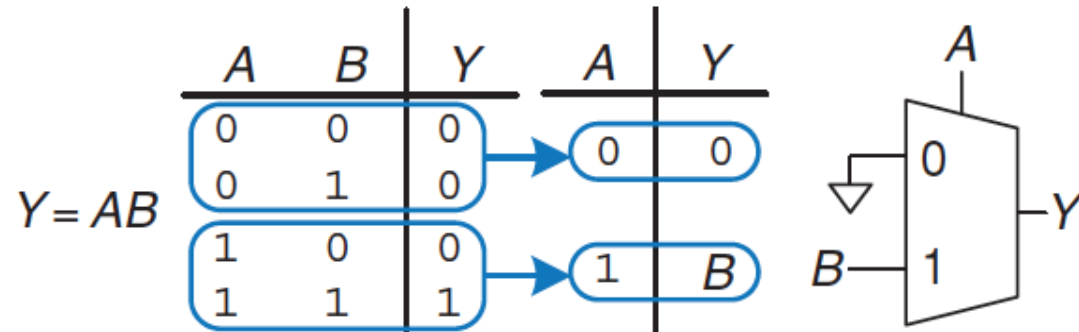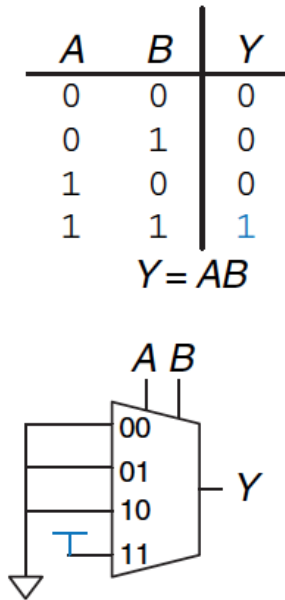

**Figure 2.59** 4:1 multiplexer implementation of two-input AND function
 
## Aside: Logic Using Multiplexers (II)

- Multiplexers can be used as lookup tables to perform logic functions






## Aside: Logic Using Multiplexers (III)

- Multiplexers can be used as lookup tables to perform logic functions

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0
 
$$Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$$




3X1 Mux

## Aside: Logic Using Multiplexers (III)

- How to implement the same logic by 2X1 MUX?

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0
 
$$Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$$




2X1 Mux

# Decoder

# Decoder



- “Input pattern detector”
- $n$  inputs and  $2^n$  outputs
- Exactly one of the outputs is 1 and all the rest are 0s
- The **one output** that is logically 1 is the output corresponding to the input **pattern** that the logic circuit is expected to detect
- Example: 2-to-4 decoder

$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 

 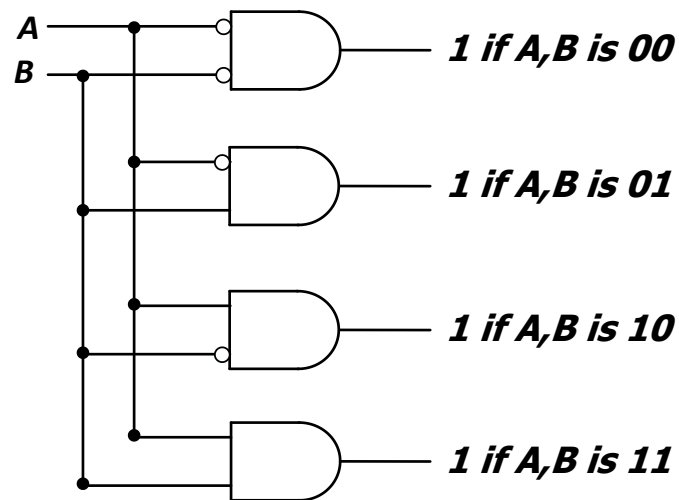
# Decoder (I)

- $n$  inputs and  $2^n$  outputs
- Exactly one of the outputs is 1 and all the rest are 0s
- The **one output** that is logically 1 is the output corresponding to the input **pattern** that the logic circuit is expected to detect


 
## Decoder (II)

- The decoder is useful in determining how to interpret a bit pattern
  - It could be the address of a row in DRAM, that the processor intends to read from
  - It could be an instruction in the program and the processor has to decide what action to do! (based on *instruction opcode*)



# Full Adder

## Full Adder (I)

- **Binary addition**
  - Similar to decimal addition
  - From right to left
  - One column at a time
  - One sum and one carry bit
- Truth table of binary addition on **one column** of bits within two n-bit operands

$$\begin{array}{r}
 a_{n-1}a_{n-2} \dots a_1a_0 \\
 b_{n-1}b_{n-2} \dots b_1b_0 \\
 \underline{C_n C_{n-1} \dots C_1} \\
 S_{n-1} \dots S_1S_0
 \end{array}$$

↓


$a_i$	$b_i$	$carry_i$	$carry_{i+1}$	$S_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


 
## Full Adder (II)

- Binary addition
  - N 1-bit additions
  - **SOP of 1-bit addition**

$$\begin{array}{r}
 a_{n-1}a_{n-2} \dots a_1a_0 \\
 b_{n-1}b_{n-2} \dots b_1b_0 \\
 \hline
 c_n c_{n-1} \dots c_1 \\
 \hline
 s_{n-1} \dots s_1s_0
 \end{array}$$




$a_i$	$b_i$	$carry_i$	$carry_{i+1}$	$S_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1




# Adder Design: Ripple Carry Adder


- Delay propagation problem

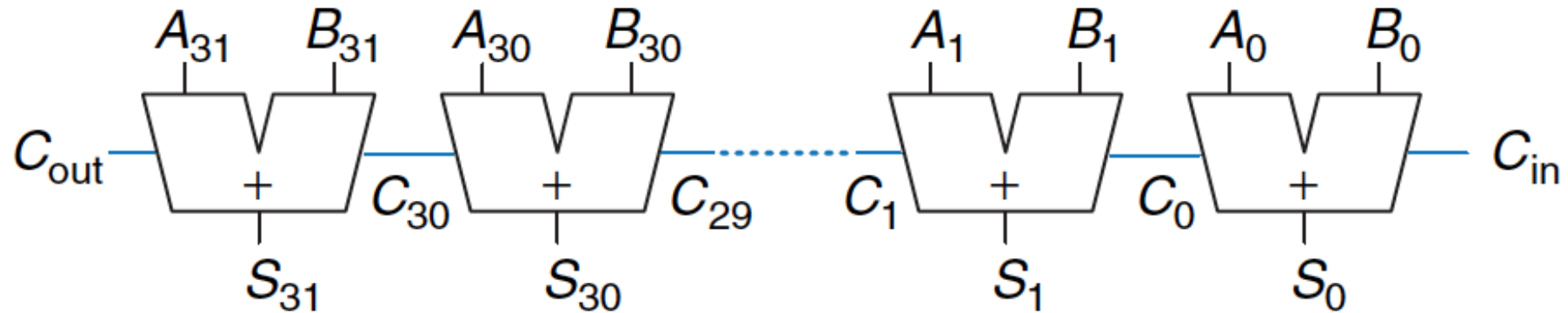

# Adder Design: Carry Lookahead Adder

 

(a)

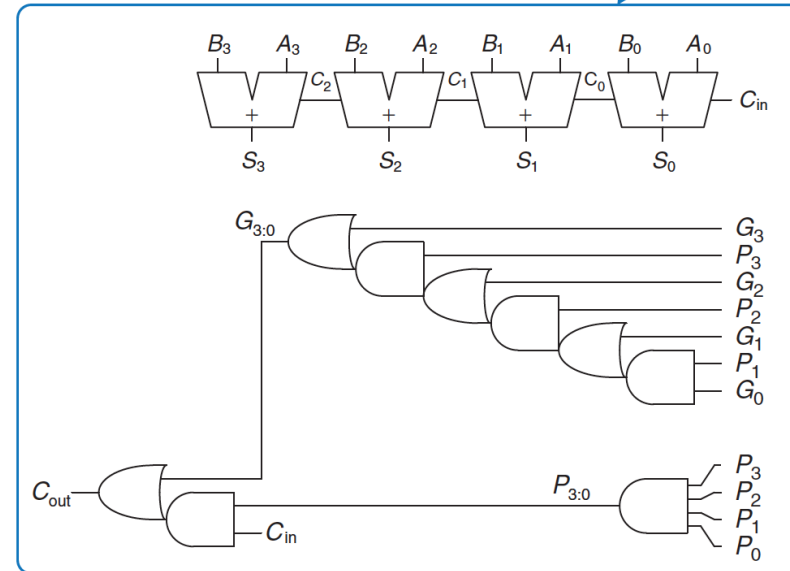


(b)

# ALU (Arithmetic Logic Unit)
 
# ALU (Arithmetic Logic Unit)

- Combines a variety of arithmetic and logical operations into a single unit (that performs only one function at a time)
- Usually denoted with this symbol:



$F_{2:0}$	Function
000	A AND B
001	A OR B
010	A + B
011	not used
100	A AND $\bar{B}$
101	A OR $\bar{B}$
110	A - B
111	SLT



# Tri-State Buffer



# Tri-State Buffer

- A tri-state buffer enables gating of different signals onto a wire
- **Floating signal (Z):** Signal that is not driven by any circuit
  - Open circuit, floating wire

 



Figure 2.40 Tristate buffer

EN	A	B	C	D	Q1	Q2	OUT
L	L	H	H	L	off	off	HI-Z
L	H	H	H	L	off	off	HI-Z
H	L	L	H	H	on	off	L
H	H	L	L	L	off	on	H

## Example: Use of Tri-State Buffers


- Imagine a wire connecting the CPU and memory
  - At any time only the CPU or the memory can place a value on the wire, both not both
  - You can have two tri-state buffers: one driven by CPU, the other memory; and ensure at most one is enabled at any time

# Example Design with Tri-State Buffers

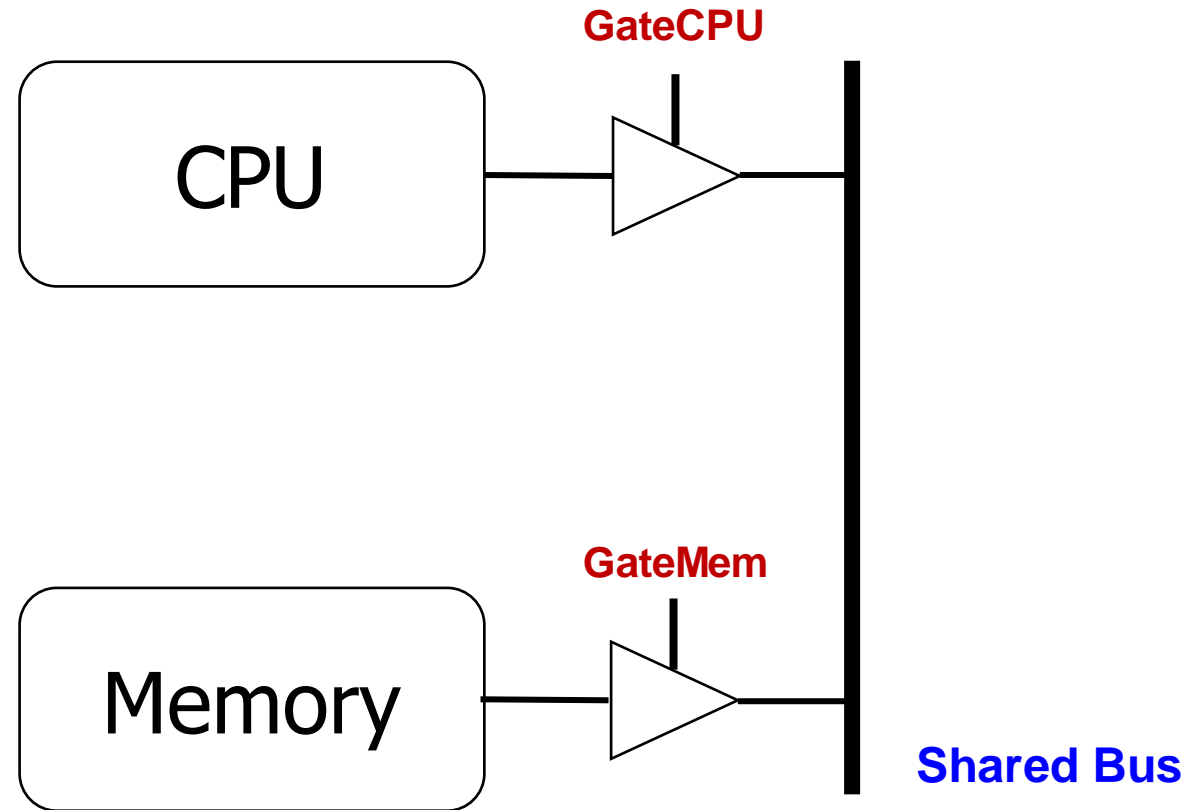

 
## Another Example


- Shared Bus is a common line between peripherals
- All of the devices connected with Tri-State Buffers
- When a device use the shared bus all other buffers are disconnected.



# Multiplexer Using Tri-State Buffers

 

**Figure 2.56** Multiplexer using tristate buffers

 

# Karnaugh Maps (K-Maps)

# Complex Cases

- One example  $C_{out} = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$
- Problem
  - **Easy** to see how to apply Uniting Theorem...
  - **Hard** to know if you applied it in all the right places...
  - ...especially in a function of many more variables
- Question
  - Is there an easier way to find potential simplifications?
  - i.e., potential applications of Uniting Theorem...?
- Answer
  - Need an intrinsically *geometric* representation for Boolean  $f( )$
  - Something we can draw, see...

# Karnaugh Map

- Karnaugh Map (K-map) method
  - K-map is an alternative method of representing the **truth table** that helps **visualize adjacencies** in up to 6 dimensions
  - Physical adjacency  $\leftrightarrow$  Logical adjacency

**2-variable K-map**

	<b>B</b>	0	1
<b>A</b>	0	00	01
	1	10	11

**3-variable K-map**

	<b>BC</b>	00	01	11	10
<b>A</b>	0	000	001	011	010
	1	100	101	111	110

**4-variable K-map**


	<b>CD</b>	00	01	11	10
<b>AB</b>	00	0000	0001	0011	0010
	01	0100	0101	0111	0110
	11	1100	1101	1111	1110
	10	1000	1001	1011	1010

**Numbering Scheme:** 00, 01, 11, 10 is called a “Gray Code” — only a *single bit (variable) changes* from one code word and the next code word



# Karnaugh Map Methods

$BC$ $A$	00	01	11	10
0	000	001	011	010
1	100	101	111	110

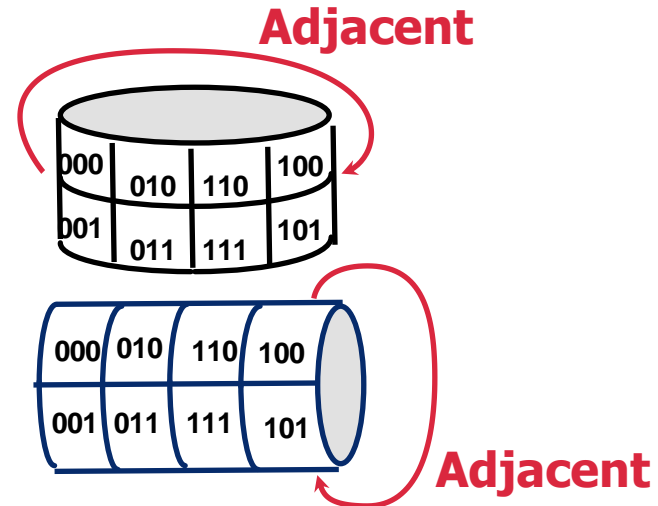

**K-map adjacencies go "around the edges"**  
**Wrap around from first to last column**  
**Wrap around from top row to bottom row**

# K-map Cover - 4 Input Variables

<i>CD</i> <i>AB</i>	00	01	11	10
00	1	0	0	1
01	0	1	0	0
11	1	1	1	1
10	1	1	1	1

$$F = A + \bar{B}\bar{D} + B\bar{C}D$$

**Strategy for "circling" rectangles on Kmap:**

**Biggest "oops!" that people forget:**


# Logic Minimization Using K-Maps

- Very simple guideline:
  - Circle all the rectangular blocks of 1's in the map, using the fewest possible number of circles
    - Each circle should be as large as possible
  - Read off the implicants that were circled
- More formally:
  - A Boolean equation is minimized when it is written as a sum of the fewest number of prime implicants
  - Each circle on the K-map represents an implicant
  - The largest possible circles are prime implicants

# K-map Rules

- **What can be legally combined (circled) in the K-map?**
  - Rectangular groups of size  $2^k$  for any integer  $k$
  - Each cell has the same value (1, for now)
  - All values must be adjacent
    - Wrap-around edge is okay
- **How does a group become a term in an expression?**
  - Determine which literals are constant, and which vary across group
  - Eliminate varying literals, then AND the constant literals
    - constant 1  $\rightarrow$  use  $X$ , constant 0  $\rightarrow$  use  $\bar{X}$
- **What is a good solution?**
  - Biggest groupings  $\rightarrow$  eliminate more variables (literals) in each term
  - Fewest groupings  $\rightarrow$  fewer terms (gates) all together
  - OR together all AND terms you create from individual groups

# K-map Example: Two-bit Comparator

 


A	B	C	D	F1	F2	F3
0	0	0	0	1	0	0
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	1	0	0
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	1	0	0
1	0	1	1	0	1	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	1	0	0

**Design Approach:**

**Write a 4-Variable K-map for each of the 3 output functions**

*K-map for F1*

 


**F1 =**

A	B	C	D	F1	F2	F3
0	0	0	0	1	0	0
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	1	0	0
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	1	0	0
1	0	1	1	0	1	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	1	0	0

# K-map Example: Two-bit Comparator (3)

*K-map for F2*

 

**F2 =**

**F3 = ? (Exercise for you)**

A	B	C	D	F1	F2	F3
0	0	0	0	1	0	0
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	1	0	0
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	1	0	0
1	0	1	1	0	1	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	1	0	0


# Sequential Logic Circuits and Design

- Circuits that can store information
  - Cross-coupled inverter
  - R-S Latch
  - Gated D Latch
  - D Flip-Flop
  - Register



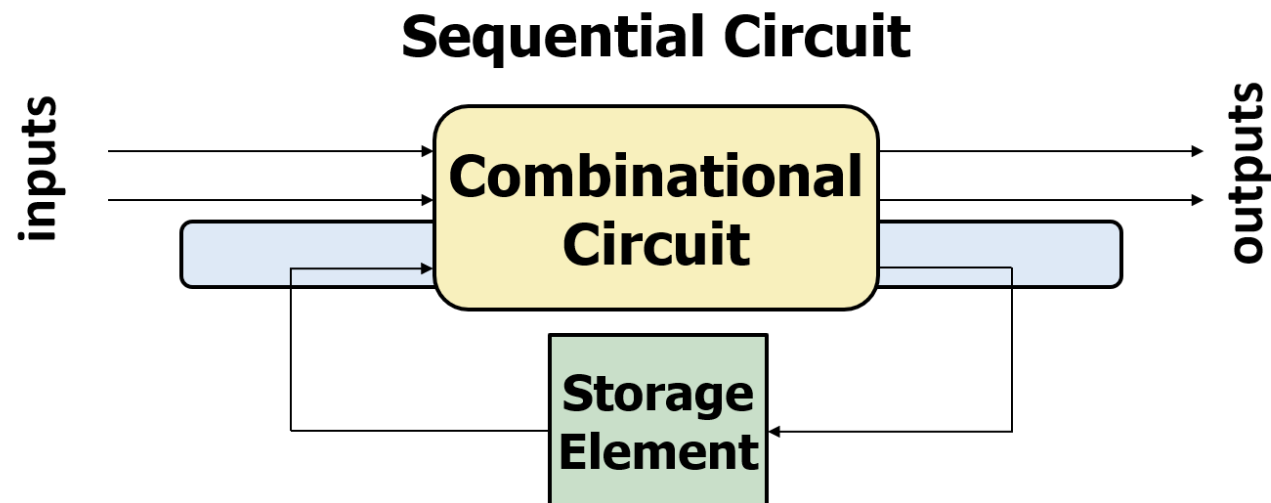
# Introduction

- Combinational circuit output depends **only** on **current** input
- We want circuits that produce output depending on **current** and **past** input values – circuits with **memory**
- How can we design a circuit that **stores information**?



# Capturing Data


# Basic Element: Cross-Coupled Inverters

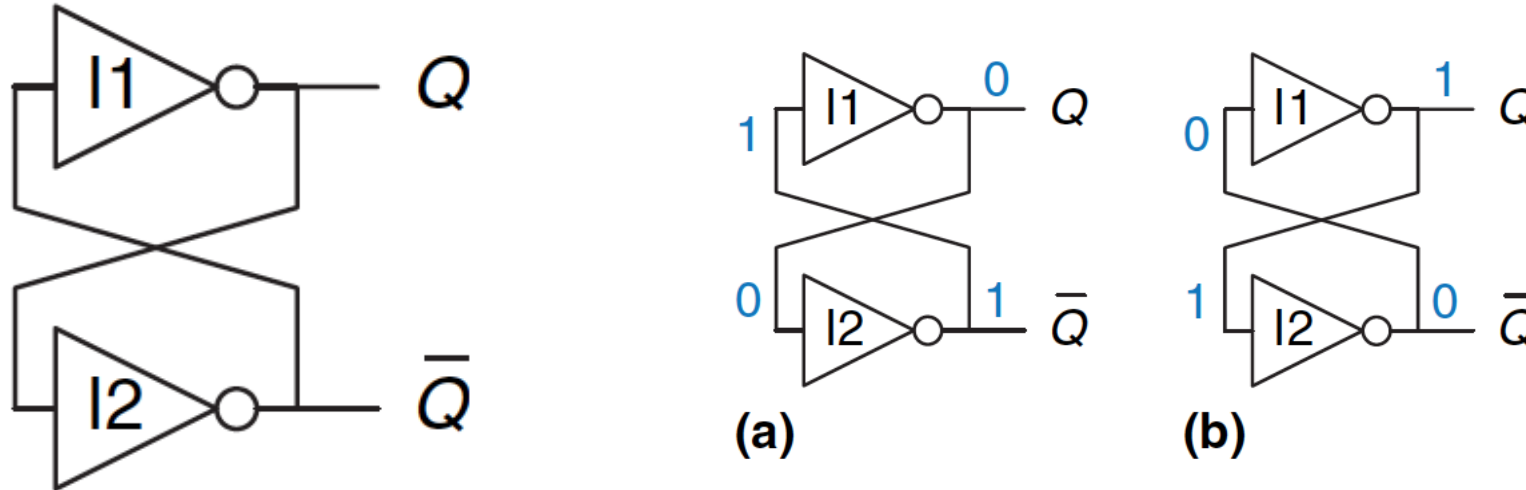

- Has two stable states:  $Q=1$  or  $Q=0$ .
- Has a third possible “metastable” state with both outputs oscillating between 0 and 1 (we will see this later)
- **Not useful without a *control mechanism* for setting  $Q$**
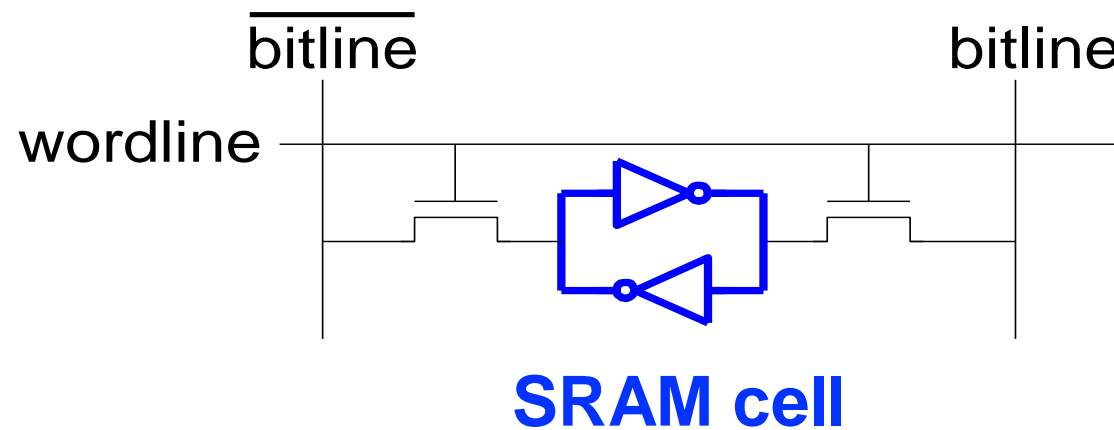
# More Realistic Storage Elements

- **Have a control mechanism for setting Q**
  - We will see the R-S latch soon
  - Let's look at an SRAM (static random access memory) cell first



- We will get back to SRAM (and DRAM) later


# The Big Picture: Storage Elements

- Latches and Flip-Flops
  - Very fast, parallel access
  - Very expensive (one bit costs tens of transistors)
- Static RAM (SRAM)
  - Relatively fast, only one data word at a time
  - Expensive (one bit costs 6+ transistors)
- Dynamic RAM (DRAM)
  - Slower, one data word at a time, reading destroys content (refresh), needs special process for manufacturing
  - Cheap (one bit costs only one transistor plus one capacitor)
- Other storage technology (flash memory, hard disk, tape)
  - Much slower, access takes a long time, non-volatile
  - Very cheap

# Basic Storage Element: The R-S Latch
 
# The R-S (Reset-Set) Latch


- Cross-coupled **NAND gates**
  - Data is stored at **Q** (inverse at **Q'**)
  - **S** and **R** are control inputs
    - In *quiescent (idle) state*, **both S and R are held at 1**
    - **S (set)**: drive **S** to 0 (keeping **R** at 1) to change **Q** to 1
    - **R (reset)**: drive **R** to 0 (keeping **S** at 1) to change **Q** to 0
- **S** and **R** should never **both** be 0 at the same time



Input		Output
R	S	Q
1	1	$Q_{\text{prev}}$
1	0	1
0	1	0
0	0	Forbidden

## Why not $R=S=0$ ?

Input		Output
R	S	Q
1	1	$Q_{\text{prev}}$
1	0	1
0	1	0
0	0	Forbidden

 


1. If  $R=S=0$ ,  $Q$  and  $Q'$  will both settle to 1, which **breaks** our invariant that  $Q = !Q'$
2. If  $S$  and  $R$  transition back to 1 at the same time,  $Q$  and  $Q'$  begin to oscillate between 1 and 0 because their final values depend on each other (**metastability**)
  - This eventually settles depending on **variation in the circuits**



# The Gated D Latch

 
# The Gated D Latch

- How do we **guarantee** correct operation of an R-S Latch?


 
# The Gated D Latch

- How do we **guarantee** correct operation of an R-S Latch?
  - Reduce the number of states to three:
    - WE/Clock = 1, D=1, Q=1
    - WE/Clock = 1, D=0, Q=0
    - WE/Clock = 0, D=X



Input		Output
WE	D	Q
0	0	$Q_{\text{prev}}$
0	1	$Q_{\text{prev}}$
1	0	0
1	1	1


- **Q** takes the value of **D**, when **write enable (WE)** is set to 1
- **S** and **R** can never be 0 at the same time!

# The Register
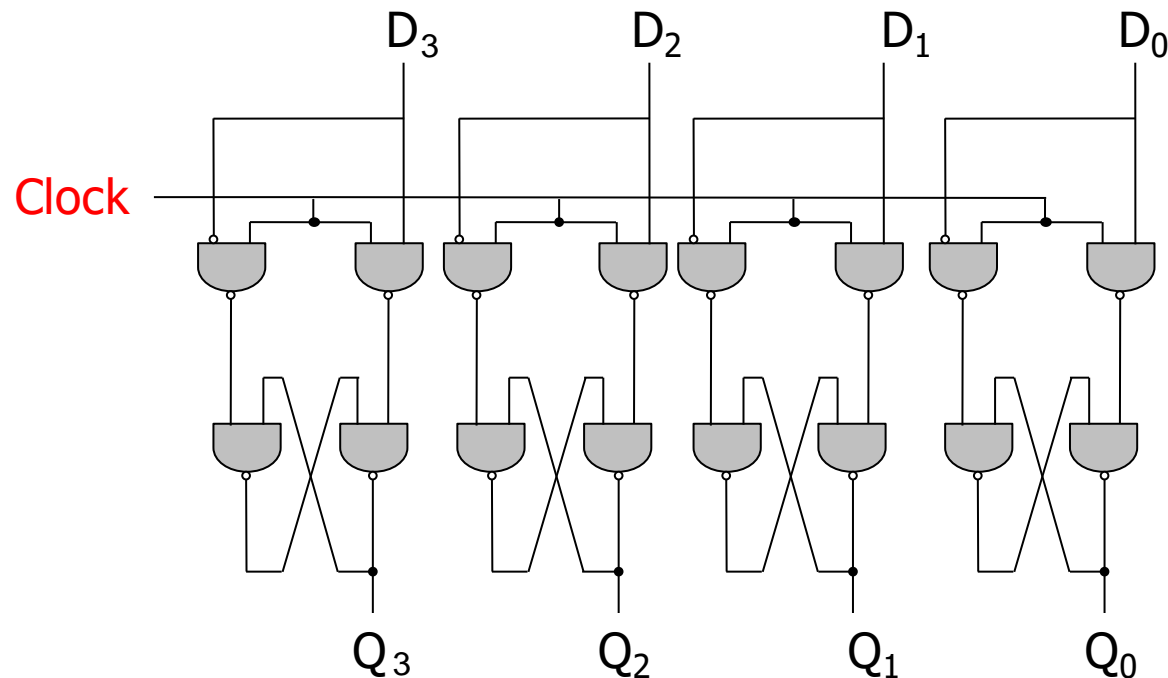
# The Register

How can we use D latches to store **more** data?

- Use **more** D latches!
- A single **Clock** signal for all latches for simultaneous writes




Here we have a **register**, or a structure that stores more than one bit and can be read from and written to

This **register** holds 4 bits, and its data is referenced as  $Q[3:0]$
 
# The Register

How can we use D latches to store **more** data?

- Use **more** D latches!
- A single **Clock** signal for all latches for simultaneous writes



Here we have a **register**, or a structure that stores more than one bit and can be read from and written to

This **register** holds 4 bits, and its data is referenced as Q[3:0]